

Class:	CPE-300L	Semester:	Spring 2020
Points		Document author:	Brysen Kokubun
		Author's email:	Brysenkokubun96@gmail.com
		Document topic:	Postlab 5
Instructor's comments:			

1. Introduction / Theory of Operation

- For this lab experiment, we implemented various FSM machines. The experiments made us create a Digital lock/unlock FSM, Model an FSM from a table, and a serial parity detector.

a. What are two types of FSMs? Explain in detail.

- Two types of FSMs are Mealy and Moore. Mealy Machine's outputs are dependent on present inputs, and current machine state. Moore machine outputs are dependent only on machines current state.

b. Write few sentences: explain how you approach designing a FSM

- The approach to take when designing a FSM is to, 1 - Choose machine type, 2 - Choose encoding style, 3 - Create Combinational logic, 4 - Create Sequential logic, 5 - Create Test bench (optional), 6 - Verify logic (Waveform, etc.)

2. Prelab Report

- Attached below

3. Experiment Results

Experiment #1: Write FSM code for digital lock & unlock

'110110' unlocks the lock any other combination will not unlock the lock

```

module digLock(clk, x0, x1, reset, z, zb, state);
    input clk, x0, x1, reset;
    output z, zb;
    reg z, zb;
    output[2:0] state;
    reg[2:0] state;
    reg[2:0] next_state;

    parameter[2:0] S0 = 3'b000;
    parameter[2:0] S1 = 3'b001;
    parameter[2:0] S2 = 3'b010;
    parameter[2:0] S3 = 3'b011;
    parameter[2:0] S4 = 3'b100;
    parameter[2:0] S5 = 3'b101;
    parameter[2:0] S6 = 3'b110;

    initial begin
        state = 3'b000;
        zb = 1'b1;
    end

    // Combinational Logic
    always @(*)
    begin
        next_state = 0;
        case(state)
            S0: begin
                z = 1'b0; // Lock
                zb = 1'b1;
            end
        end
    end

```

Verilog Code for Digital Lock

```

        if ((x0 == 1'b1) || (reset == 1'b1)) begin
            next_state = S0;
        end else if (x1 == 1'b1) begin
            next_state = S1;
        end
        else next_state = S0;
    end

    S1: if (x0 == 1'b1 || reset == 1'b1) begin
        next_state = S0;
    end else if (x1 == 1'b1) begin
        next_state = S2;
    end
    else next_state = S1;

    S2: if (x1 == 1'b1 || reset == 1'b1) begin
        next_state = S0;
    end else if (x0 == 1'b1) begin
        next_state = S3;
    end else next_state = S2;

    S3: if (x0 == 1'b1 || reset == 1'b1) begin
        next_state = S0;
    end else if (x1 == 1'b1) begin
        next_state = S4;
    end else next_state = S3;

    S4: if (x0 == 1'b1 || reset == 1'b1) begin
        next_state = S0;
    end else if (x1 == 1'b1) begin
        next_state = S5;
    end else next_state = S4;

    S5: if (x1 == 1'b1 || reset == 1'b1) begin
        next_state = S0;
    end else if (x0 == 1'b1) begin
        next_state = S6;
    end else next_state = S6;

    S6: begin
        z = 1'b1; // Unlock
        zb = 1'b0;
        if (reset == 1'b1)
            next_state = S0;
        else next_state = S6;
    end
endcase
end

// Sequential Logic
always @(posedge clk)
begin
    state <= #1 next_state;
end

endmodule


module onehertz(clk_50mhz, clk_1hz);
input clk_50mhz;
output clk_1hz;
reg clk_1hz;
reg [24:0] count;
always @ (posedge clk_50mhz)
begin
    if(count == 24999999) begin
        count <= 0;
        $dumpfile("f.vcd");
        clk_1hz <= ~clk_1hz;
    end
    else begin
        count <= count + 1;
    end
end
endmodule

```

DE2 Board Implementation

L – Signifies Lock

U – Signifies Unlock

 

Experiment #2: Model FSM machine: FSM Model's Table's logic

FSM Verilog Code

```
module fsm(clk, x, reset, z, state);
    input clk, x, reset;
    output z;
    reg z;
    output[2:0] state;
    reg[2:0] state;
    reg[2:0] next_state;

    parameter[2:0] S0 = 3'b000;
    parameter[2:0] S1 = 3'b001;
    parameter[2:0] S2 = 3'b010;
    parameter[2:0] S3 = 3'b011;
    parameter[2:0] S4 = 3'b100;
    parameter[2:0] S5 = 3'b101;
    parameter[2:0] S6 = 3'b110;

    initial begin
        state = 3'b000;
    end

    // Combinational Logic
    always @(*)
    begin
        next_state = 0;
        case(state)
            S0: begin
                z = 1'b0; // Lock
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = S1;
                    z = 1'b1;
                end else begin
                    next_state = S2;
                    z = 1'b0;
                end
            end
            S1: begin
                z = 1'b1;
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = S0;
                end else begin
                    next_state = S3;
                end
            end
            S2: begin
                z = 1'b0;
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = S4;
                end else begin
                    next_state = S5;
                end
            end
            S3: begin
                z = 1'b1;
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = S1;
                end else begin
                    next_state = S6;
                end
            end
            S4: begin
                z = 1'b1;
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = S0;
                end else begin
                    next_state = S5;
                end
            end
            S5: begin
                z = 1'b0;
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = S2;
                end else begin
                    next_state = S6;
                end
            end
            S6: begin
                z = 1'b0;
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = S4;
                end else begin
                    next_state = S3;
                end
            end
        endcase
    end
end
```

PS	NS		Z	
	X=0	X=1	X=0	X=1
S ₀	S ₁	S ₂	1	0
S ₁	S ₃	S ₄	1	0
S ₂	S ₄	S ₄	0	1
S ₃	S ₅	S ₅	0	1
S ₄	S ₅	S ₆	1	0
S ₅	S ₀	S ₀	0	1
S ₆	S ₀	-	1	-

```

S1: if (x == 1'b0 || reset == 1'b1) begin
    next_state = S3;
    z = 1'b1;
end else begin
    next_state = S4;
    z = 1'b0;
end

S2: if (x == 1'b0 || reset == 1'b1) begin
    next_state = S4;
    z = 1'b0;
end else begin
    next_state = S4;
    z = 1'b1;
end

S3: if (x == 1'b0 || reset == 1'b1) begin
    next_state = S5;
    z = 1'b0;
end else begin
    next_state = S5;
    z = 1'b1;
end

S4: if (x == 1'b0 || reset == 1'b1) begin
    next_state = S5;
    z = 1'b1;
end else begin
    next_state = S6;
    z = 1'b0;
end

S5: if (x == 1'b0 || reset == 1'b1) begin
    next_state = S0;
    z = 1'b0;
end else begin
    next_state = S0;
    z = 1'b1;
end

S6: if (x == 1'b0 || reset == 1'b1) begin
    next_state = S0;
    z = 1'b1;
end else begin
    next_state = S6;
    z = 1'b1;
end

endcase
end

// Sequential Logic
always @(posedge clk)
begin
    state <= #1 next_state;
end

endmodule

```

FSM Test Bench

Verilog Code

Timing diagram for fsm_tb showing signals /fsm_tb/dk, /fsm_tb/x, /fsm_tb/reset, /fsm_tb/z, and /fsm_tb(u0)/state over time. The diagram shows a sequence of state transitions triggered by reset and data changes.

Experiment #3: Design Serial parity detector

Parity indicates whether the number of '1's is odd or even. '1' indicates odd, '0' indicates even

```

module bitDetect(clk, x, reset, z, state);
    input clk, x, reset;
    output z;
    reg z;
    output state;
    reg state;
    reg next_state;

    parameter E = 0;
    parameter O = 1;

    initial begin
        state = 0;
    end

    // Combinational Logic
    always @(*)
    begin
        next_state = 0;
        case(state)
            E: begin
                if ((x == 1'b0) || (reset == 1'b1)) begin
                    next_state = E;
                    z = 1'b0;
                end else if ((x == 1'b1) || (reset == 1'b0)) begin
                    next_state = O;
                end
            end
            O: if (x == 1'b0 || reset == 1'b0) begin
                next_state = O;
                z = 1'b1;
            end else if (x == 1'b1 || reset == 1'b1) begin
                next_state = E;
            end
        endcase
    end

    // Sequential Logic
    always @(posedge clk)
    begin
        state <= #1 next_state;
    end

endmodule

```

Serial parity detector Verilog Code

```

module bitDetect_tb;

    reg x, clk, reset;
    wire z;

    initial begin
        clk = 0;
        #5 reset = 1;
        #5 reset = 0;
        x = 1;
    end


    always begin
        #2 clk = ~clk;
        #500;
        x = 0;
    end

    bitDetect TB(clk, x, reset, z, state);
endmodule

```

Serial parity detector Test Bench Code

Serial parity detector Waveform

 

4. Questions

1. What is the difference between mealy and moore machine?

Mealy machine outputs are dependent on present inputs, and current machine state. Moore machine outputs are dependent only on machines current state.

2. What is encoding style in a FSM?

There are many styles to encode a FSM, One hot, Binary, Gray, One cold, etc. Encoding is a way to assign unique patterns of zeros and ones to the defined states of a Finite State Machine.

3. What is a combinational section and sequential section in a FSM design used for?

The combinational section of an FSM is designed for the next state logic of the FSM. Combinational section is modeled using functions, assignment statements or case statements. The sequential section of an FSM is designed for the state registers and output logic. Sequential section is modeled using only edge sensitive logic such as always block w/posedge or negedge of clock.

5. Conclusions

- To conclude this lab experiment, we learned how to properly create a FSM for the given experiments. We learned about the two types of FSMs, Mealy and Moore and how they differ. This Lab allowed us to create the FSM for a digital lock, Modeling a FSM from a table, and create a FSM for a serial parity bit detector. We did not really encounter any problems for this lab, a possible problem could be that we ran out of time in the scheduled lab hours. In order to resolve this problem, my partner and I met together outside of the scheduled lab hours to finish any unfinished experiments. Overall this lab taught us the steps to take, necessary logic, and design techniques are needed in order to create a Finite State Machine.

Class:	CPE-300L	Semester:	Spring 2020
Points		Document author:	Brysen Kokubun
		Author's email:	Brysenkokubun96@gmail.com
		Document topic:	Prelab 5
Instructor's comments:			

Introduction / Theory of operation


- For this lab experiment we will be learning about Finite State Machines. There are two types of machines that we will be implementing, Mealy and Moore machines. Mealy machines outputs are dependent on present inputs, and current state while Moore machines outputs are dependent only on machines current state. This lab will teach us about FSM components, design and how to implement those designs as waveforms and on DE2 boards.

Prelab main content

1. What is a Finite State Machine? What are the components in a FSM?

- A Finite State Machine is a computation model (software/hardware) that is used to simulate sequential logic. Also, the FSM can only be in one state at any given time. The components in a FSM are sets of states, transitions between states, and actions associated with each transition (entering, exiting or remaining in a state).

2. Digital lock design

 

3. Read modeling FSM (Chapter 14)

Introduction to FSM

State machine or FSM are the heart of any digital design, of course counter is a simple form of FSM. When I was learning Verilog, I use to wonder "How do I code FSM in Verilog" and "What is the best way to code it". I will try to answer the first part of the question below and second part of the question could be found in the tidbits section.