

Class:	CPE-300L	Semester:	Spring 2020
Points		Document author:	Brysen Kokubun
		Author's email:	Brysenkokubun96@gmail.com
		Document topic:	Prelab 4
Instructor's comments:			

Introduction / Theory of operation

- For this lab experiment we will be implementing various latches and flip-flops, Verilog models, synchronous and asynchronous operation and asynchronous system design. We will be verifying our models by using the RTL viewer, Waveforms and DE2 board implementations.


Prelab main content

1. Implementation of SR latch: Structural Verilog Models

<pre> 1 module part1 (clk, R, S, Q); 2 input clk, R, S; 3 output Q; 4 wire R_g, S_g, Qa, Qb; 5 6 assign R_g = R & clk; 7 assign S_g = S & clk; 8 assign Qa = ~(R_g Qb); 9 assign Qb = ~(S_g Qa); 10 assign Q = Qa; 11 12 endmodule 13 </pre>	<pre> 1 module part1 (clk, R, S, Q); 2 input clk, R, S; 3 output Q; 4 wire R_g, S_g, Qa, Qb; 5 and (R_g, R, clk); 6 and (S_g, S, clk); 7 nor (Qa, R_g, Qb); 8 nor (Qb, S_g, Qa); 9 assign Q = Qa; 10 endmodule 11 </pre>
--	---

Component Instantiation

Structural Model

 

Waveforms of both modules created the same output. The difference between the 2 codes are the way they are written. One code uses component instantiation with assign statements and another code uses a structural model with gate primitives. Both will perform same task just written differently.


2. Asynchronous set/clear

```

1 module part1 (clk, D, set, clear, Q);
2     input clk, D, set, clear;
3     output Q;
4     wire R_g, S_g, Qa, Qb, S, R;
5
6     assign R = ~D;
7     assign S = D;
8     nand (R_g, R, clk);
9     nand (S_g, S, clk);
10    nand (Qb, ~set, S_g, Qa);
11    nand (Qa, ~clear, R_g, Qb);
12    assign Q = Qb;
13
14 endmodule
15

```

S-R latch with added set and clear input

 

3. JK flip-flop

JK #1

```

module J_K (Q, QN, J, K, Clock);
    output Q, QN; //data output
    input J, K; //data input
    input Clock;
    reg Q;
    always @(posedge Clock)
    begin
        Q = J & (~Q) | (~K) & Q;
    end
    assign QN = ~Q;
endmodule

```

JK #2

```

module J_K (Q, QN, J, K, Clock);
    output Q, QN; //data output
    input J, K; //data input
    input Clock;
    reg Q;
    always @(posedge Clock)
    begin
        if ({J,K} == 2'b01) Q = 1'b0;
        else if ({J,K} == 2'b10) Q = 1'b1;
        else if ({J,K} == 2'b11) Q = ~Q;
        else Q = Q;
    end
    assign QN = ~Q;
endmodule

```


JK #3

```

module J_K (Q, QN, J, K, Clock);
    output Q, QN; //data output
    input J, K; //data input
    input Clock;
    reg Q;
    always @(posedge Clock)
    begin
        case ({J,K})
            2'b01: Q = 1'b0;
            2'b10: Q = 1'b1;
            2'b11: Q = ~Q;
            default: Q = Q;
        endcase
    end
    assign QN = ~Q;
endmodule

```

Waveforms

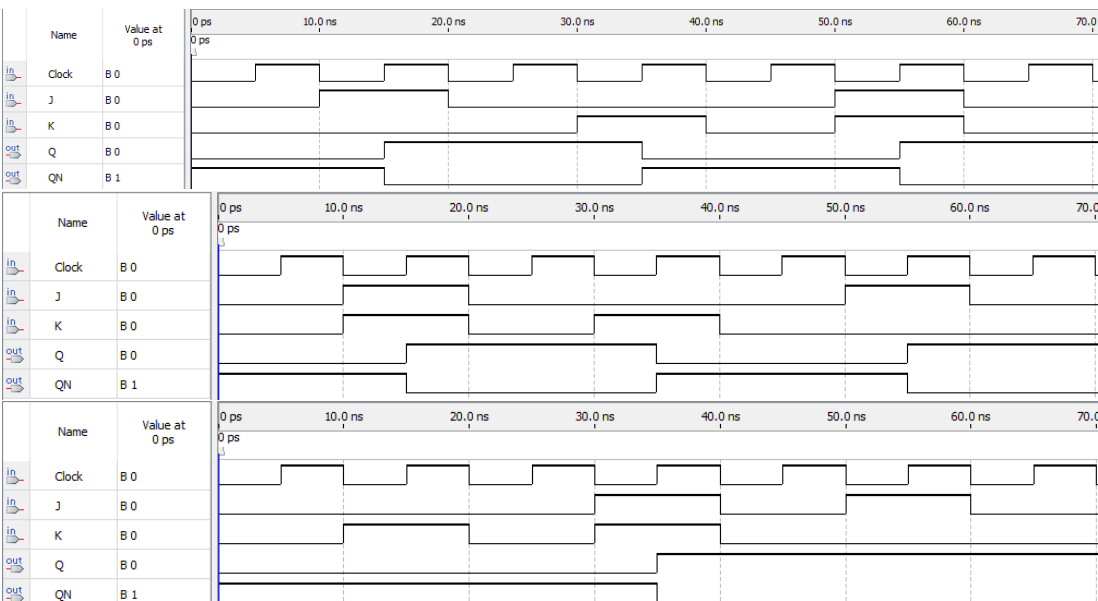

JK #1

JK #2

JK #3

Utilization

JK #1

JK #2

JK #3

Resource Usage Summary		Resource Usage Summary		Resource Usage Summary	
Resource	Usage	Resource	Usage	Resource	Usage
▼ Total logic elements	1 / 14,400 (< 1 %)	▼ Total logic elements	1 / 14,400 (< 1 %)	▼ Total logic elements	1 / 14,400 (< 1 %)
-- Combinational with no register	0	-- Combinational with no register	0	-- Combinational with no register	0
-- Register only	0	-- Register only	0	-- Register only	0
-- Combinational with a register	1	-- Combinational with a register	1	-- Combinational with a register	1
▼ Logic element usage by number of LUT inputs		▼ Logic element usage by number of LUT inputs		▼ Logic element usage by number of LUT inputs	
-- 4 input functions	0	-- 4 input functions	0	-- 4 input functions	0
-- 3 input functions	1	-- 3 input functions	1	-- 3 input functions	1
-- <=2 input functions	0	-- <=2 input functions	0	-- <=2 input functions	0
-- Register only	0	-- Register only	0	-- Register only	0
▼ Logic elements by mode		▼ Logic elements by mode		▼ Logic elements by mode	
-- normal mode	1	-- normal mode	1	-- normal mode	1
-- arithmetic mode	0	-- arithmetic mode	0	-- arithmetic mode	0
▼ Total registers*	1 / 14,733 (< 1 %)	▼ Total registers*	1 / 14,733 (< 1 %)	▼ Total registers*	1 / 14,733 (< 1 %)
-- Dedicated logic registers	1 / 14,400 (< 1 %)	-- Dedicated logic registers	1 / 14,400 (< 1 %)	-- Dedicated logic registers	1 / 14,400 (< 1 %)
-- I/O registers	0 / 333 (0 %)	-- I/O registers	0 / 333 (0 %)	-- I/O registers	0 / 333 (0 %)
Total LABs: partially or completely used	1 / 900 (< 1 %)	Total LABs: partially or completely used	1 / 900 (< 1 %)	Total LABs: partially or completely used	1 / 900 (< 1 %)
Virtual pins	0	Virtual pins	0	Virtual pins	0
▼ I/O pins	5 / 81 (6 %)	▼ I/O pins	5 / 81 (6 %)	▼ I/O pins	5 / 81 (6 %)
-- Clock pins	0 / 6 (0 %)	-- Clock pins	0 / 6 (0 %)	-- Clock pins	0 / 6 (0 %)
-- Dedicated input pins	0 / 12 (0 %)	-- Dedicated input pins	0 / 12 (0 %)	-- Dedicated input pins	0 / 12 (0 %)
Global signals	0	Global signals	0	Global signals	0
M9Ks	0 / 60 (0 %)	M9Ks	0 / 60 (0 %)	M9Ks	0 / 60 (0 %)
Total block memory bits	0 / 552,960 (0 %)	Total block memory bits	0 / 552,960 (0 %)	Total block memory bits	0 / 552,960 (0 %)
Total block memory implementation bits	0 / 552,960 (0 %)	Total block memory implementation bits	0 / 552,960 (0 %)	Total block memory implementation bits	0 / 552,960 (0 %)
PLLS	0 / 3 (0 %)	PLLS	0 / 3 (0 %)	PLLS	0 / 3 (0 %)

4. JK with synchronous clear

```

1  module J_K (Q, QN, J, K, ClearN, Clock);
2      output Q, QN;           //Output Data
3      input J, K, ClearN;    //Input Data
4      input Clock;
5      reg Q;
6      always @(posedge Clock)
7      begin
8          case ({J,K,ClearN})
9              3'bxx0: Q = 1'b0;
10             3'b011: Q = 1'b0;
11             3'b101: Q = 1'b1;
12             3'b111: Q = ~Q;
13             default: Q = Q;
14         endcase
15     end
16     assign QN = ~Q;
17 endmodule

```

