

Class:	CPE-300L	Semester:	Spring 2020
Points		Document author:	Brysen Kokubun
		Author's email:	Brysenkokubun96@gmail.com
		Document topic:	Postlab 3
Instructor's comments:			

1. Introduction / Theory of Operation

- Lab experiment #3 familiarize with ModelSim and its software for testbenches. We will also be reviewing and designing combinational circuits. Some of the circuits being designed are Ripple adder, ALU, implementing 7-seg on DE2 board, and Comparator.

1. What is the mega function in Quartus? List applications.
 - Mega function is a black box containing a logic design. The mega function can be used as an instantiation of other functions in a design file and inputs are parameters to the function.
2. What is continuous assignment and procedural assignment in Verilog?
 - Continuous assignments are structural logic connections and can be used to symbolize combinational logic. Procedural assignments simply assign values to variables, registers, etc.

2. Prelab


- Attached

3. Experiment Results

Experiment #1: 7-Segment in Verilog

- Wrote Verilog code to use 7-segment on the DE2 board using toggle switches.

```
1 module segmentDisplay(switch,display);
2     input[3:0] switch;
3     output[6:0] display;
4     reg[6:0] display;
5
6     always@(*)
7     case(switch)
8         4'b0000: display = 7'b1000000; // 0
9         4'b0001: display = 7'b1111001; // 1
10        4'b0010: display = 7'b0100100; // 2
11        4'b0011: display = 7'b0110000; // 3
12        4'b0100: display = 7'b0011001; // 4
13        4'b0101: display = 7'b0010010; // 5
14        4'b0110: display = 7'b0000010; // 6
15        4'b0111: display = 7'b1111000; // 7
16        4'b1000: display = 7'b0000000; // 8
17        4'b1001: display = 7'b0010000; // 9
18        default: display = 7'b1000000; // Default 0
19    endcase
20 endmodule
```

 

Here are 2 examples of 7-segment on DE2 board 4 = 0100, second 3 = 0011.

Experiment #2: Magnitude Comparator from prelab 3

- Comparing two 1-bit values for magnitude. 3 cases $a < b$, $a = b$, $a > b$

Verilog Code

```
module Comparator(a, b, less, eq, greater);
    input a, b;
    output less, eq, greater;
    wire y1, y2;
    not F1(y1, a);
    not F2(y2, b);
    and F3(less, y1, b);
    and F4(greater, y2, a);
    xnor F5(eq, a, b);
endmodule
```


```
module comp_tb;
    reg a, b;
    wire less, greater, eq;
```

```
    Comparator G1 (
        .a (a),
        .b (b),
        .less (less),
        .greater (greater),
        .eq (eq)
    );
```

```
    initial begin
        a = 0;
        b = 0;
        #10
        a = 0;
        b = 1;
        #10
        a = 1;
        b = 0;
        #10
        a = 1;
        b = 1;
        #10
        a = 0;
        b = 0;
        end
endmodule
```

Test Bench Code

Waveform

 

- 00 equal to (Middle LED ON)
- 01 less than (Left LED ON)
- 10 greater than (Right LED ON)
- 11 equal to (Middle LED ON)

- Designed a 3-bit ripple adder and implemented on the DE2 board with 7-segment

Test Bench Code

```

module rippleAdderTB;
    reg [2:0] A, B;
    reg CIN;
    wire [3:0] SUM;

    initial begin
        CIN = 0;

        A[0] = 0;
        A[1] = 0;
        A[2] = 0;
        B[0] = 1;
        B[1] = 0;
        B[2] = 1;
        #10

        A[0] = 1;
        A[1] = 0;
        A[2] = 0;
        B[0] = 1;
        B[1] = 1;
        B[2] = 1;
        #10


        A[0] = 0;
        A[1] = 1;
        A[2] = 0;
        B[0] = 1;
        B[1] = 1;
        B[2] = 1;
        #10

        A[0] = 1;
        A[1] = 1;
        A[2] = 0;
        B[0] = 0;
        B[1] = 1;
        B[2] = 1;
        #10

        A[0] = 1;
        A[1] = 1;
        A[2] = 1;
        B[0] = 0;
        B[1] = 0;
        B[2] = 0;

        end
    rippleAdder RA(A,B,CIN,SUM);
endmodule

```

 

Here are 2 examples of the outputs from the RippleAdder on the DE2 board.

- 4-bit ALU with 8 opcodes of operations

```

1
2 module ALU(A, B, Cin, out, Cout, control);
3     input[3:0] A;        // First operand 4 bits
4     input[3:0] B;        // Second operand
5     input Cin;           // Carry in
6     output[3:0] out;     // Output 4 bits
7     reg [3:0] out;
8     output Cout;         // Carry out
9     reg Cout;
10    input[2:0] control;   // Select signals
11
12    always@(*)
13    begin
14        case(control)     // 3 signals = 2^3 operations = 8
15            3'b000: out = A & B;        // AND operation
16            3'b001: out = A | B;        // OR operation
17            3'b010: out = {A[0], A[3], A[2], A[1]}; // Rotate A right
18            3'b011: assign {Cout,out} = A+B+Cin; // Add
19            3'b100: assign {Cout,out} = A-B-Cin; // Subtract
20            3'b101: out = {A[2], A[1], A[0], A[3]}; // Rotate A left
21            3'b110: out = {1'b0, A[3], A[2], A[1]}; // Shift Right, shift in 0
22            3'b111: out = {A[2], A[1], A[0], 1'b0}; // Shift Left, shift in 0
23
24        endcase
25    end
26 endmodule

```

[illegible]

4. Questions

1. Why ModelSim is better than Quartus internal simulator?
 - Both ModelSim and Quartus can run simulations but ModelSim is created more for simulation and testing of projects while Quartus is used more for configurations and programming devices.
2. How does initial block differ from always block?
 - The initial block only runs once during program execution and the always block will always run in order to check for signal changes.
3. What is the difference between \$finish and \$stop in Verilog testbench?
 - Finish will complete the testbench code and stop will stop the testbench code in its position.

5. Encountered Problems

- For this lab experiment we had difficulty applying our Verilog code to assign to certain pins on the 7-seg display on the DE2 board. But after writing out the logic, we were able to correctly pin assign. Also, some of the labs do not have the proper version of Quartus installed which created an issue of where we could work on the experiment at school.

6. Conclusions

- To conclude this lab, we used both Quartus and ModelSim to compile, simulate, and create waveforms for our experiments. We successfully created and implemented a comparator, Ripple adder, and ALU. We were able to create testbenches to easily see outputs on waveforms. We also implemented our Verilog codes on the DE2 boards 7-seg and switches. This lab helped us get a better handling of Quartus and ModelSim and what type of functions they have to offer.